

MICROPROCESSOR LAB EXPERIMENT 2

Deenabandhan N ee23b021
Sai Harshith Gajendra ee23b069
Krutarth Patel ee23b137

14 August 2024

Introduction

FPGA board : Edge Artix 7

This experiment involves

- Simulating a half-adder using Xilinx Vivado and implementing on the FPGA board.
- Extending the half-adder design to a full-adder, simulating it and implementing on the FPGA board.
- Designing a 4-bit ripple-carry adder and implementing on the FPGA board.

Xilinx Vivado

- We were introduced to Xilinx vivado , a software that is used to synthesize and analyse the hardware description designs.
- The procedures that we followed are ,
 - Create a project with source file as our Verilog code.
 - Add constraints to the ports that we have defined in the Verilog code.
 - Run the synthesis to check whether our Verilog code has any error in it.
 - We can open the Schematics to see the design that we have coded in Verilog.
 - After running synthesis , we can run simulation using our testbench and check for logical errors.
 - Once we confirm there is no logical/syntax error , we can run the implementation which basically implements our hardware description in the board which we have chosen while creating the project.
 - After the implementation is done , we can generate bitstream which is basically a file that contains the configuration information for an FPGA.
 - Once we successfully generate the bitstream , we can connect the target source and program it with the generated bitstream.
- In this report , we have included
 - Verilog code for module instantiation.
 - We have included both data flow as well as gate level modelling here.
 - The Schematics generated from Xilinx Vivado.
 - The Constraints file generated for FPGA.
 - The testbench and simulation generated
 - The analysis of reports obtained from Xilinx Vivado.

DFlipflop

Aim :

- The aim of this part of experiment is to stimulate a D-Flip flop using Verilog code.
- We have just stimulated in verilog and not implemented it in FPGA. This will be used in the following part of Johnson counter.
- We have used behavioural model to stimulate it and used positive edge of the clock to trigger the flip flop.
- We have tried out two different possibilities of reset button.
 - The reset button can be used as an asynchronous button with negative edge triggered i.e when reset goes from 1 to 0 irrespective of the clock position , it resets to zero.
 - The reset button can be used as a synchronous button which resets only when the clock is positive edge triggered.

Code for synchronous reset

```
module D_FF(input D,clk,rst,output Q,Qbar);
    reg Q,Qbar;
    always@(posedge clk)
    begin
        if(rst==1'b0)
        begin
            Q=0;
            Qbar=1;
        end
        else
        begin
            Q<=D;
            Qbar<=(~(D));
        end
    end
endmodule
```

Schematics for synchronous reset

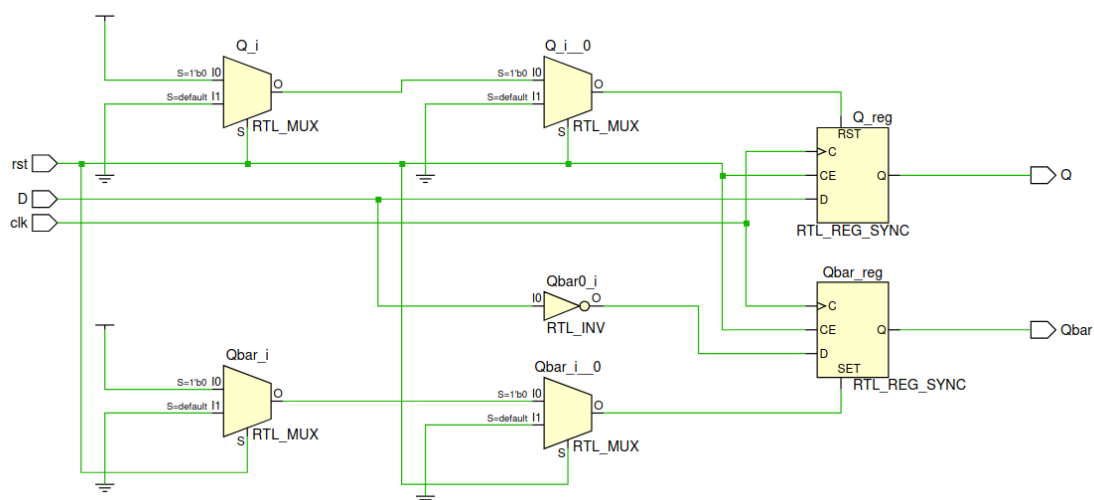


Figure 1: Schematics of the D-Flipflop with synchronous reset

Code for asynchronous reset

```

module D_FF(input D,clk,rst,output Q,Qbar);
    reg Q,Qbar;
    always@(posedge clk , negedge rst)
    begin
        if(rst==1'b0)
        begin
            Q=0;
            Qbar=1;
        end
        else
        begin
            Q<=D;
            Qbar<=(~(D));
        end
    end
end
endmodule

```

Schematics for Asynchronous reset

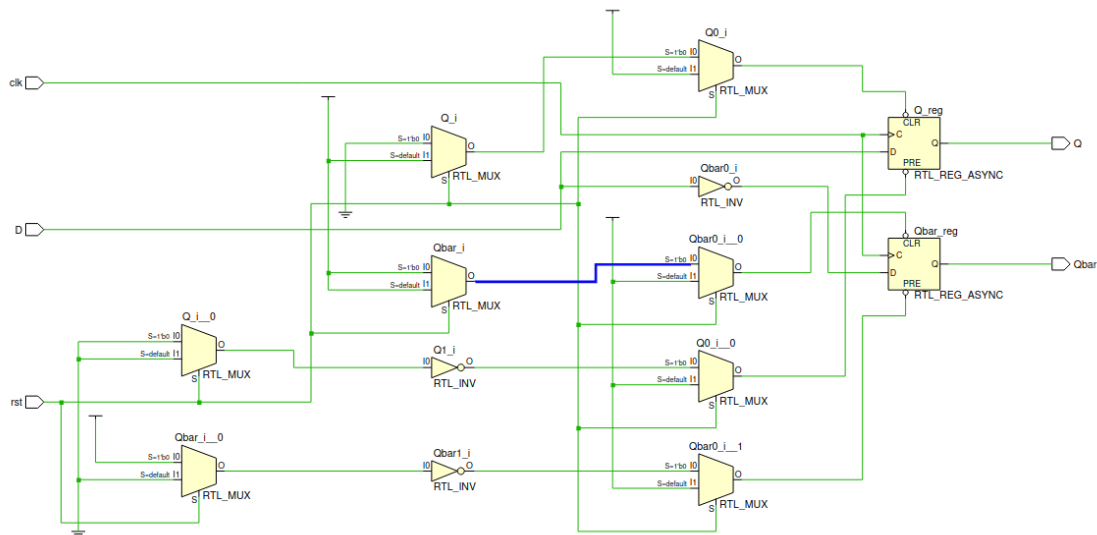


Figure 2: Schematics of the D-Flipflop with asynchronous reset

Testbench

```

`timescale 1ns/100ps

module test;
    reg clk,reset,D;
    wire Q,Q_bar;

    D_FF d(D,clk,reset,Q,Q_bar);

    initial
    begin
        clk=0;reset=1;D=0;
        #10 reset=0; // This negative edge trigger will cause initial values to get assigned to 0
        #20 reset=1;
        repeat(40) // The number of cycles
        begin
            #10 clk=~(clk); // Inverting the clock pulse
        end
    end
end

```


```

initial
begin
    #5;
    repeat(20)
        #20 D=~(D);

    #20 $finish;
end
endmodule

```

Simulation

 

Clock Divider

```
module clk_gen(input clk,reset,output out);
    reg out;
    reg [3:0] count=0;

    always@(posedge clk or negedge reset)
    begin
        if(reset==1'b0)
        begin
            out=0;
            count=0;

        end
        else
        begin
            count+=1;
            if(count==5)
            begin
                out=~(out);
                count=0;
            end
        end
    end
end
endmodule
```

Johnson Counter

Behavioral Model

```
module decoder(input [2:0] cntr,output [7:0] led);
    reg [6:0] val;
    assign led={1'b1,~(val)};

    always@(cntr)
    begin
        case(cntr)
            3'd0 : val=7'b0111111;
            3'd1 : val=7'b0000110;
            3'd2 : val=7'b1011011;
            3'd3 : val=7'b1001111;
            3'd4 : val=7'b1100110;
            3'd5 : val=7'b1101101;
            3'd6 : val=7'b1111101;
            3'd7 : val=7'b0000111;
        endcase
    end
endmodule

module Johnson_count(input clk_in,reset,input [3:0] digit,output [7:0] led);
    wire [2:0] cntr;
    wire q0,q1,q2;
    wire q0_bar,q1_bar,q2_bar;
    wire clk_out;

    assign digit=4'b0001;

    clk_gen c1(clk_in,reset,clk_out);

    D_FF d1(q0_bar,clk_out,reset,q2,q2_bar);
    D_FF d2(q2,clk_out,reset,q1,q1_bar);
    D_FF d3(q1,clk_out,reset,q0,q0_bar);

    assign cntr={q2,q1,q0};

    decoder de1(cntr,led);

endmodule
```

Schematics :

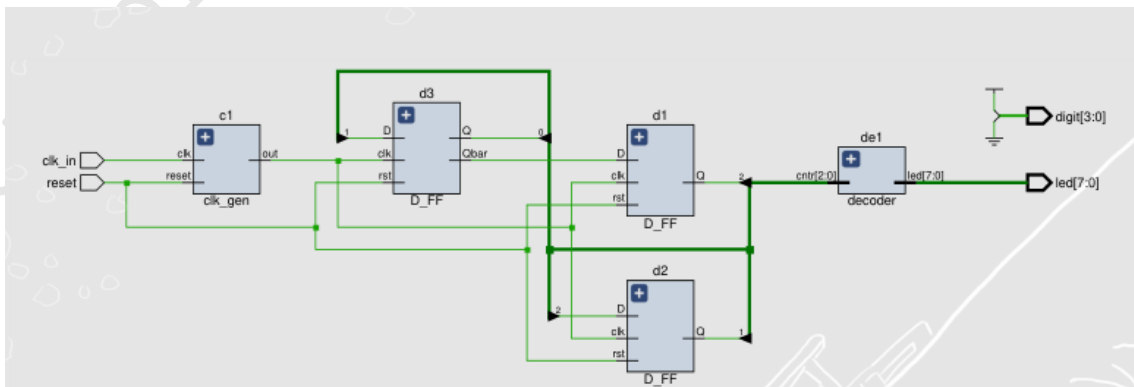


Figure 3: Schematics of the Johnson Counter

Testbench


```
module test;
    reg clk,reset;
    wire [7:0] out;
    wire [3:0] digit;
    assign digit = 4'b0001;
    Johnson_count d(clk, reset, digit, out);

    initial
    begin
        clk=0;reset=1;
        #10 reset=0;
        #20 reset=1;
        repeat(80)
        begin
            #10 clk=~(clk);
        end
    end
    initial
    begin
        #820 $finish;
    end
endmodule
```

Constraints on ports of FPGA

```
set_property IOSTANDARD LVCMOS33 [get_ports {digit[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {digit[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {digit[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {digit[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {led[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {led[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {led[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {led[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {led[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {led[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {led[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {led[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports clk_in]
set_property IOSTANDARD LVCMOS33 [get_ports reset]
set_property PACKAGE_PIN F2 [get_ports {digit[0]}]
set_property PACKAGE_PIN E1 [get_ports {digit[1]}]
set_property PACKAGE_PIN G5 [get_ports {digit[2]}]
set_property PACKAGE_PIN G4 [get_ports {digit[3]}]
set_property PACKAGE_PIN H1 [get_ports {led[7]}]
set_property PACKAGE_PIN H2 [get_ports {led[6]}]
set_property PACKAGE_PIN J4 [get_ports {led[5]}]
set_property PACKAGE_PIN J5 [get_ports {led[4]}]
set_property PACKAGE_PIN H4 [get_ports {led[3]}]
set_property PACKAGE_PIN H5 [get_ports {led[2]}]
set_property PACKAGE_PIN G1 [get_ports {led[1]}]
set_property PACKAGE_PIN G2 [get_ports {led[0]}]
set_property PACKAGE_PIN N11 [get_ports clk_in]
set_property PACKAGE_PIN L5 [get_ports reset]
```

Simulation :

 

Reports :

Resources utilized :

- 47 **SLICE LUT** were used, where LUT is used as a logic and not memory.
- 37 Slice Registers were used as Flip Flop.

Clock :

- only 1 Global Clock was utilized.

<i>Clock Region Name</i>	<i>Global Clock (Used)</i>	FF (Used)	LUTM (Used)
<i>X0Y0</i>	<i>0</i>	<i>0</i>	<i>0</i>
<i>X1Y0</i>	<i>0</i>	<i>0</i>	<i>0</i>
<i>X0Y1</i>	<i>0</i>	<i>0</i>	<i>0</i>
<i>X1Y1</i>	<i>1</i>	<i>37</i>	<i>6</i>
<i>X0Y2</i>	<i>0</i>	<i>0</i>	<i>0</i>
<i>X1Y2</i>	<i>0</i>	<i>0</i>	<i>0</i>

Time delays

<i>Type of Path</i>	<i>Path taken</i>	Time delay (ns)
<i>Min Delay path</i>	d3 → d1	<i>0.220</i>
	d2 → d3	<i>0.368</i>
	d1 → d2	<i>0.376</i>
<i>Max Delay path</i>	c1/count_reg[5] → c1/count_reg[29]	<i>8.051</i>
	c1/count_reg[5] → c1/count_reg[31]	<i>8.030</i>
	c1/count_reg[5] → c1/count_reg[30]	<i>7.956</i>

Power consumed

- The power consumed by FPGA is **0.325W**